

(a) By reference to an amplifier, explain what is meant by *negative feedback*.

fraction of V_{out} that is sent back to the V^- input

[2]

(b) An amplifier circuit incorporating an ideal operational amplifier (op-amp) is shown in Fig. 10.1.

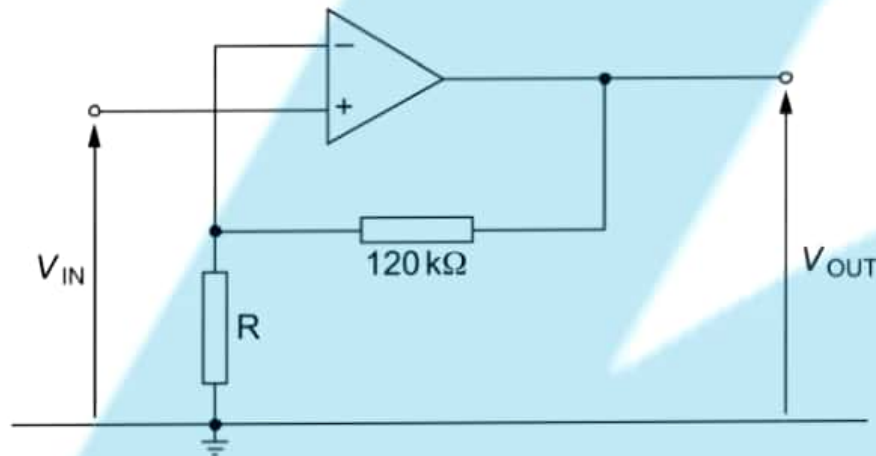


Fig. 10.1

The supply for the op-amp is $\pm 9.0\text{V}$.
The amplifier circuit is to have a gain of 25.

Calculate the resistance of resistor R.

$$1 + \frac{R_f}{R_{in}} = 25$$

$$1 + \frac{120}{R_{in}} = 25$$

$$1 - 25 = -\frac{120}{R_{in}}$$

$$R_{in} = \frac{-120}{-24} = 5\text{ k}\Omega$$

resistance = ~~9800~~ $5000\ \Omega$ [2]

(c) State the value of the output voltage V_{OUT} of the amplifier in (b) for input voltages V_{IN} of

(i) -0.08V ,

$$25(-0.08 - 0)$$

$V_{OUT} = -2\text{ V}$ [1]

(ii) $+0.4\text{V}$.

$$25(0.4)$$

$V_{OUT} = 9\text{ V}$ [1]

An amplifier incorporating an operational amplifier (op-amp) has three inputs A, B and C, as shown in Fig. 9.1.

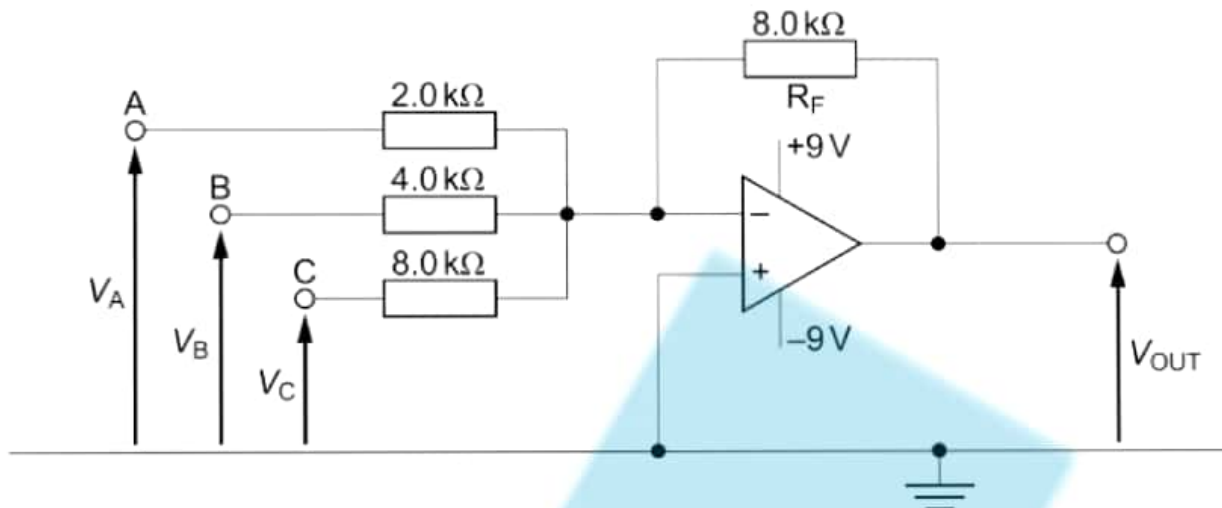


Fig. 9.1

Negative feedback is provided by the resistor R_F of resistance $8.0\text{ k}\Omega$.

For each of the inputs A, B and C, the amplifier may be considered as a single input amplifier. That is, each input is independent of the other two.

When the amplifier is not saturated, the output potential V_{OUT} is given by the expression

$$V_{OUT} = -(4V_A + GV_B + V_C),$$

where V_A , V_B and V_C are the input potentials of the inputs A, B and C respectively and G is a constant.

(a) State two effects of negative feedback on an amplifier.

1. *Reduces V_{out} , makes it less likely it would saturate*
2. *Reduces the gain, greater stability*

- (b) In the expression for the output potential V_{OUT} , the constant G is the gain associated with input B. Show that the numerical value of G is 2.

$$\text{gain} = \frac{R_f}{R_{in}} = \frac{8}{4} = 2$$

[1]

- (c) The input potentials V_A , V_B and V_C are either zero or 1.0V.

The magnitudes of some output potentials for different combinations of V_A , V_B and V_C are shown in Fig. 9.2.

V_A/V	V_B/V	V_C/V	V_{OUT}/V
0	0	1	1
0	1	0	..2.. -3.
1	0	0	4
1	0	1	5
1	1	0	..6..
1	1	1	..7..

Fig. 9.2 - $(4(0) + 2(1) + 0)$

- (i) Complete Fig. 9.2 for the three remaining values of V_{OUT} .
- (ii) Suggest a use for this circuit.

DAC

[1]

[1]

The circuit of Fig. 10.1 may be used to indicate temperature change.

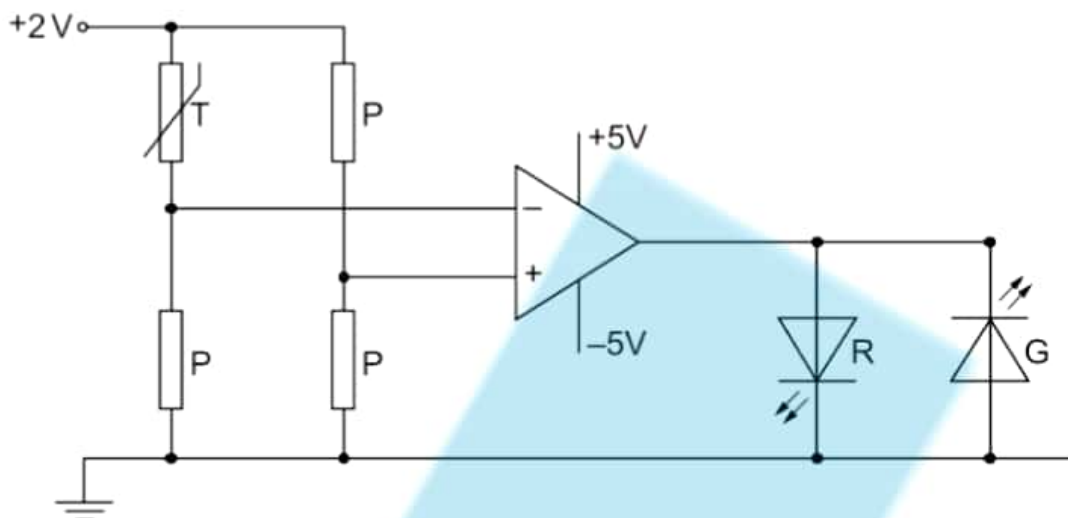


Fig. 10.1

The resistance of the thermistor T at 16°C is 2100Ω and at 18°C, the resistance is 1900Ω. Each resistor P has a resistance of 2000Ω.

Determine the change in the states of the light-emitting diodes R and G as the temperature of the thermistor changes from 16°C to 18°C.

$$V_{out} \text{ at } 16^{\circ}\text{C} = 9 \left[\left(\frac{2 \times 2}{2+2} \right) - \left(\frac{2 \times 2}{2+2.1} \right) \right]$$

$$= 9(1 - 0.975)$$

$$= +ve$$

$$V_{out} \text{ at } 18^{\circ}\text{C} = 9 \left[\left(\frac{2 \times 2}{2+2} \right) - \left(\frac{2 \times 2}{2+1.9} \right) \right]$$

$$= 9(1 - 1.025)$$

$$= -ve$$

when 16°C, R is on, G is off. then as temp goes to 18°C, R turns off, green turns on.

[4]

An amplifier circuit incorporating an operational amplifier (op-amp) is shown in Fig. 9.1.

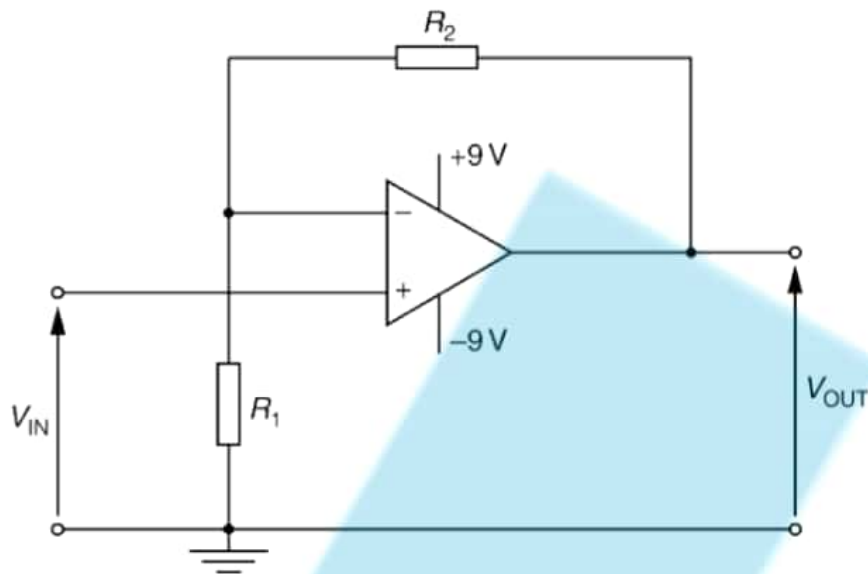


Fig. 9.1

(a) State

(i) the name of this type of amplifier circuit,

..... non inverting [1]

(ii) the gain G in terms of resistances R_1 and R_2 .

..... $G = 1 + \frac{R_2}{R_1}$ [1]

(b) The value of R_1 is $820\ \Omega$. The resistor of resistance R_2 is replaced with a light-dependent resistor (LDR).

The input potential difference V_{IN} is 15 mV .

Calculate the output potential difference V_{OUT} for the LDR having a resistance of

(i) $100\ \Omega$ (the LDR is in sunlight),

$$\text{gain} = 1 + \frac{R_2}{R_1} = 0.12195$$

$$V_{out} = 0.12195 (15 \times 10^{-3} - 0) = 0.017$$

$$V_{OUT} = 0.017 \text{ V} [1]$$

(ii) $1.0\text{ M}\Omega$ (the LDR is in darkness).

$$\text{gain} = 1 + \frac{1 \times 10^6}{820} = 1220.5$$

$$= 1220.5 (15 \times 10^{-3} - 0) = 18.3 \text{ V}$$

$$V_{OUT} = +9 \text{ V} [1]$$

An operational amplifier (op-amp) may be used as part of the processing unit in an electronic sensor.

(a) State three properties of an ideal op-amp.

1. *gain \propto*
2. *infinite input impedance*
3. *zero output impedance*

[3]

(b) A comparator circuit incorporating an ideal op-amp is shown in Fig. 9.1.

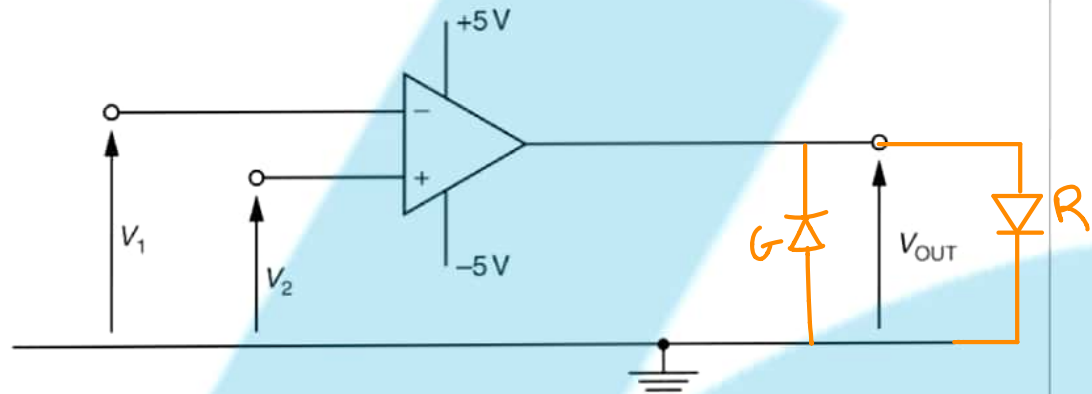


Fig. 9.1

$$V_{out} = 2(1.5 - 1.5)$$

(i) In one application of the comparator, V_2 is kept constant at +1.5V. The variation with time t of the potential V_1 is shown in Fig. 9.2. The potential V_2 is also shown.

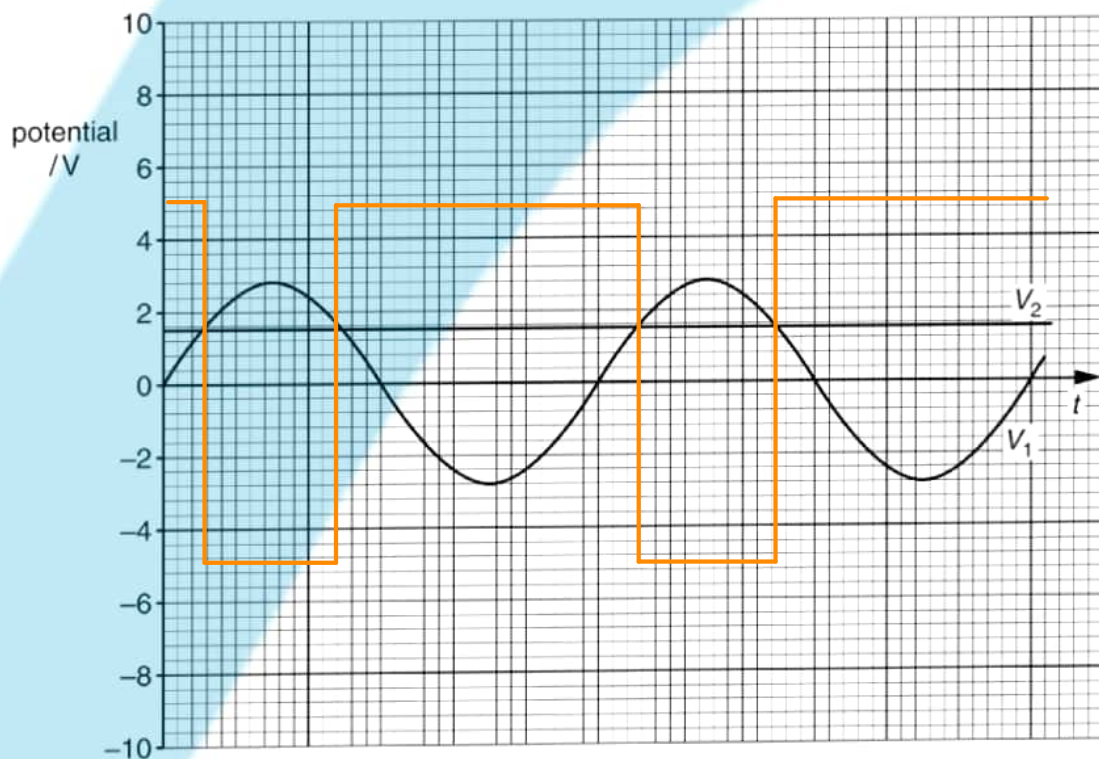


Fig. 9.2

On Fig. 9.2, show the variation with time t of the output potential V_{OUT} .

[4]

(ii) Two light-emitting diodes (LEDs) R and G are connected to the output of the op-amp in Fig. 9.1 such that R emits light for a longer time than G.

On Fig. 9.1, draw the symbols for the two diodes connected to the output of the op-amp and label the diodes R and G.

[3]

(a) State three properties of an ideal operational amplifier (op-amp).

1. *infinite input impedance*
2. *infinite gain*
3. *infinite bandwidth*

[3]

(b) An amplifier circuit is shown in Fig. 9.1.

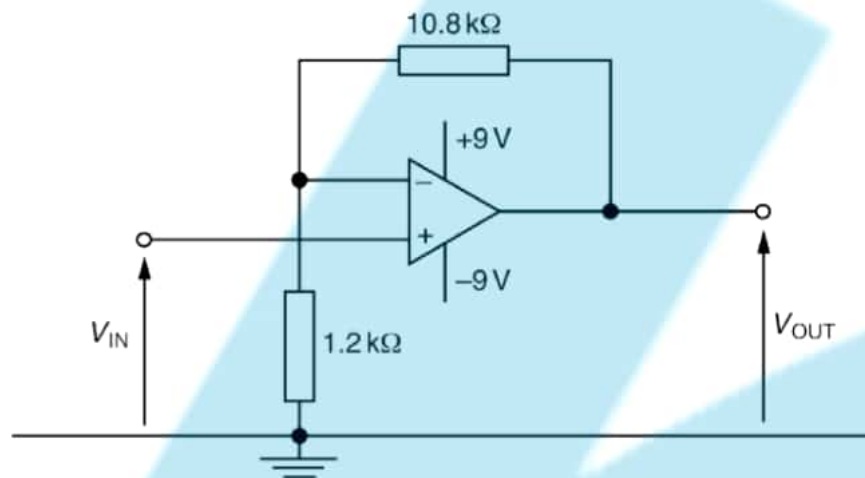


Fig. 9.1

(i) Calculate the gain of the amplifier circuit.

$$1 + \frac{10.8}{1.2} = 10$$

gain = *10* [2]

(ii) The variation with time t of the input potential V_{IN} is shown in Fig. 9.2.

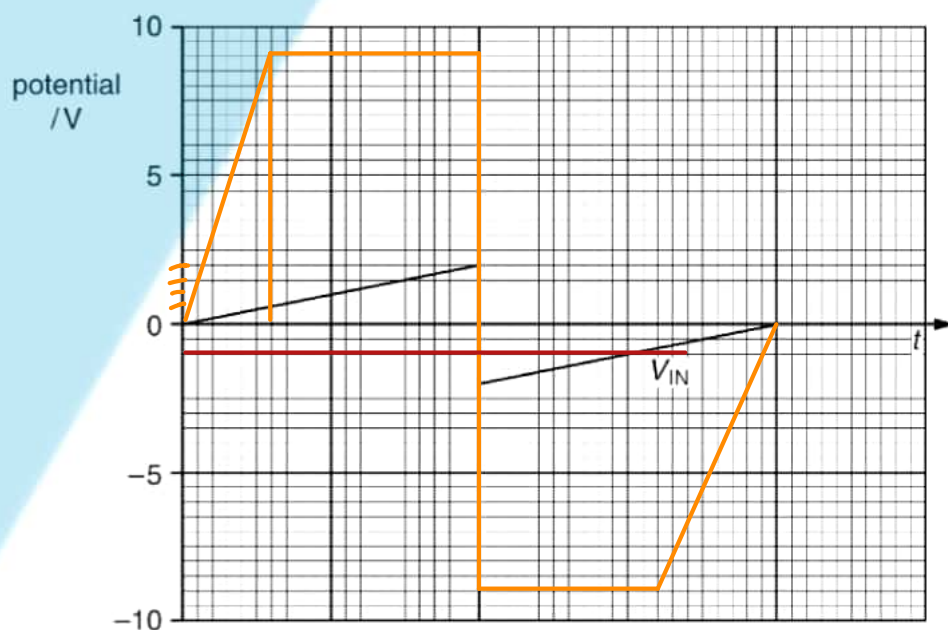


Fig. 9.2

On the axes of Fig. 9.2, show the variation with time t of the output potential V_{OUT} .

$$q = 10(x) \\ 0.9 \\ 10(0.9) = 9$$